

Application Note 2:

Using the Xgen as a Constant Current Source

Normal operation of the Xgen power supply is as a constant (or user controlled) voltage source. To use the Xgen as a constant current source, the following circuit should be implemented.

